



iW3616(7) Blsense Resistor Selection Guide Rev. 1

iWatt Inc
675 Campbell Technology Parkway, Suite 150
Campbell, CA 95008
USA

Table of Contents

1.0. Introduction	3
2.0. BJT Gain Detection	4
3.0. Blsense Resistor	5
4.0. Summary	5

1.0 Introduction

iW3616 and iW3617 are the third generation phase-cut dimmable LED driver controllers. Their two-stage architecture provides smooth dimming experience and minimizes the output current ripple. Its power factor correction (PFC) stage uniquely utilizes the bipolar power transistor (BJT) as the main power switch. The BJT also performs the bleeding function when it works with a phase-cut dimmer. iWatt's patented BJT current gain detection technology allows the BJT safe operation in the linear mode.

Figure 1 shows a typical application circuit with iW3616. The PFC stage includes boost inductor L3, main switch Q2, rectifier D3, boost output capacitor C3 and current sense resistor R6. The boost current sense signal is directly connected to the Blsense pin (Pin 3) of the controller. During the initial power-on, there is a 30ms dimmer detection time. Q2 works in linear mode to load the dimmer with constant current. In order to operate Q2 safely, the DC current gain of Q2 is measured before applying the driving current. Once the dimmer detection completes, Q2 operates in switching mode or linear mode depends on the input condition.

If there is no dimmer detected, the boost converter

operates in power factor correction mode. Q2 works as a power switch. If a phase-cut dimmer is detected, then Q2 works in both the switching mode and the linear mode depending on the dimming status. Because the current gain of the BJT varies by temperature, the driving current needs to adapt to this gain variation in order to provide consistent bleeding current. iW3616 and iW3617 have a built-in gain detection algorithm to measure the gain and control the bleeding current to within the BJT safe operating range. In the LED driver design, the BJT bleeding current can be optimized by the selection of the Blsense resistor. The Blsense resistor impacts the dimming control, the boost switching over-current protection and the Vcc loading. This guide discusses the BJT control methodology and how to select the Blsense resistor.

This design guide first explains the current gain detection and bleeding current control. Then the Blsense resistor selection section calculates the Blsense resistor based on the bleeding function requirements, as well as discuss the impacts to over-current protection threshold and Vcc loading.

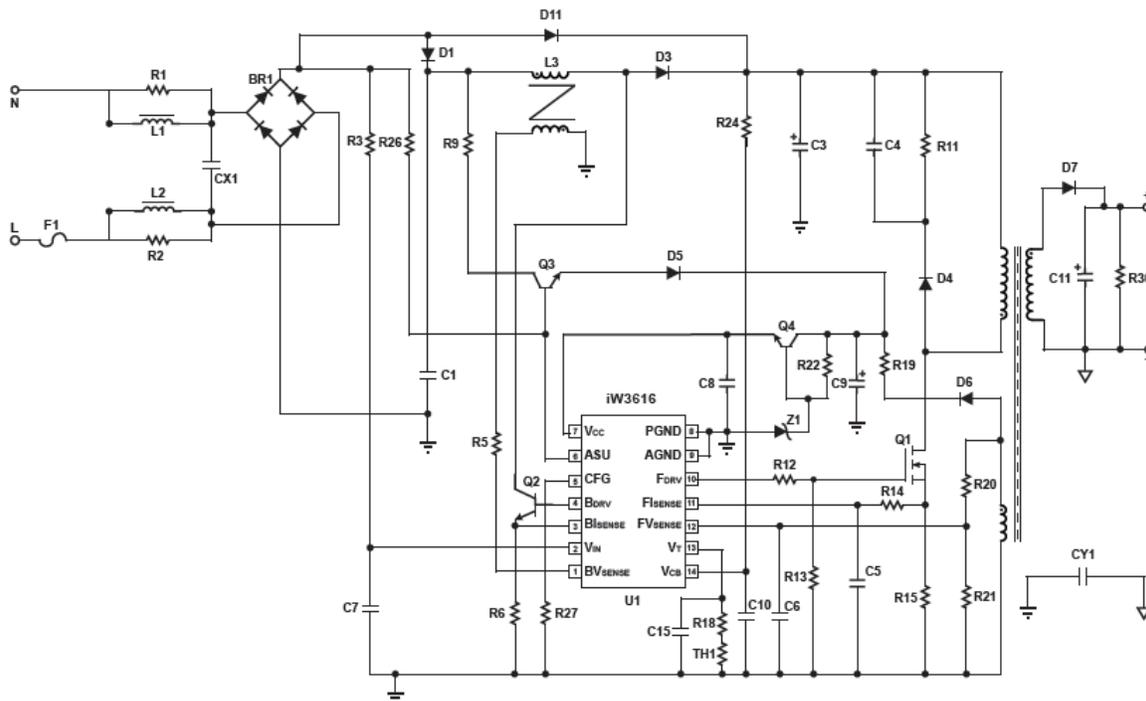


Fig. 1 Typical Application Schematic

2.0 BJT Gain Detection

Figure 2 shows the BJT control diagram. The BJT driver sends out the Q2 base drive current I_b based on the drive command. The current sense resistor R6 is connected between the emitter of Q2 and ground. The emitter current sense voltage Blsense is compared with the window comparators with thresholds of $V_{reg_th(Hi)}$ and $V_{reg_th(Lo)}$ for current gain detection. During the detection time, the control logic continuously increases or reduces the base drive current such that the emitter current sense voltage can settle between $V_{reg_th(Hi)}$ and $V_{reg_th(Lo)}$.


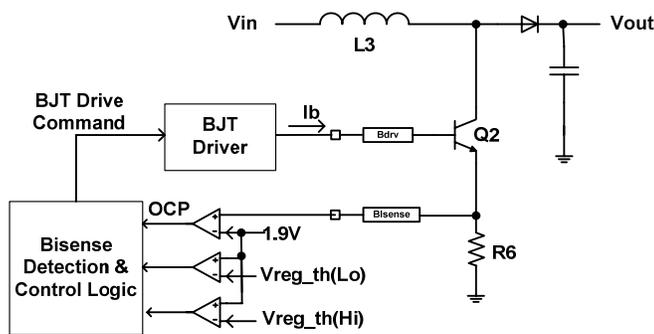


Fig. 2 BJT control blockdiagram


Figure 3 shows an example of the BJT gain detection process. The clock period is 16us. Assume in CLK1 I_b current is low, the current sense Blsense falls below $V_{reg_th(Lo)}$. The control logic decides to increase the I_b current in CLK2. During CLK2, Figure 3 illustrates an example that I_b is too high and the Blsense rises above $V_{reg_th(Hi)}$. In CLK3, the control logic further reduces the drive current with a smaller step and the Blsense falls within the threshold window of $V_{reg_th(Hi)}$ and $V_{reg_th(Lo)}$. Since Blsense settles within the target window of $V_{reg_th(Hi)}$ and $V_{reg_th(Lo)}$, in CLK4, the control logic no longer increases or reduces the I_b current. The BJT gain is then known to the controller. It is equal to $(V_{Blsense}/R6)/I_b - 1$. Two notes:

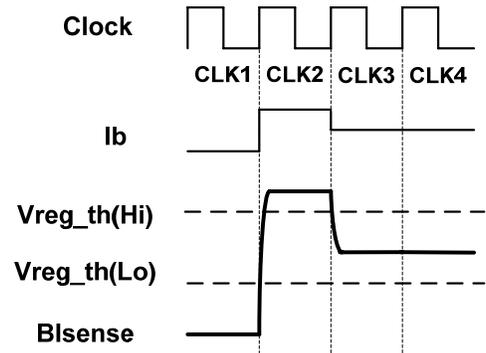- 1) In this calculation, the controller does not attempt to know the exact current gain value. Only the target I_b current is recorded. Therefore, the user can adjust R6 to change the controller's target bleeding current level.
- 2) The BJT drive current is recorded when the

Blsense voltage settles between $V_{reg_th(Hi)}$ and $V_{reg_th(Lo)}$. Although it is possible to find more accurate value, it is not required for the proper operation of iW3616 and iW3617 circuits.



(a) Illustration diagram

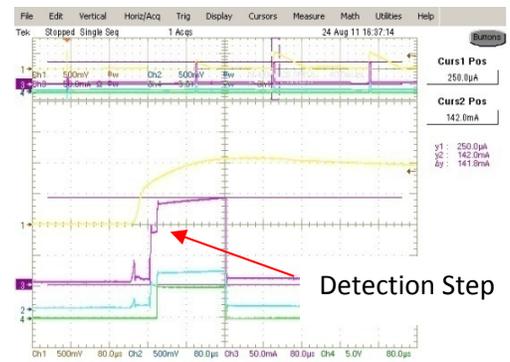

(b) Waveform

Ch1: Vin sense ; Ch2: Blsense; Ch3: Ib

Fig. 3 BJT gain detection

The current gain detection process is initiated under three conditions:

- 1) During the power-on dimmer detection time, the gain detection process is initiated when the V_{in} sense voltage rises above 0.14V.
- 2) If a leading edge dimmer is detected, the gain detection process is initiated for every half AC cycle. The process starts when the rising edge of the V_{in} sense goes above 0.14V.
- 3) If a trailing edge dimmer is detected, the gain detection process is initiated for every 32 half AC cycles. The process starts when the rising edge of the V_{in} sense goes above 0.21V.

Trademark Information

© 2012 iWatt Inc. All rights reserved. iWatt, BroadLED, **EZ-EMI**, Flickerless, Intelligent AC-DC and LED Power, and PrimAccurate are trademarks of iWatt Inc. All other trademarks and registered trademarks are the property of their respective owners.

Contact Information

Web: <https://www.iwatt.com>

E-mail: info@iwatt.com

Phone: +1 (408) 374-4200

Fax: +1 (408) 341-0455

iWatt Inc.

675 Campbell Technology Parkway, Suite 150
Campbell, CA 95008

Disclaimer and Legal Notices

iWatt reserves the right to make changes to its products and to discontinue products without notice. The applications information, schematic diagrams, and other reference information included herein is provided as a design aid only and are therefore provided as-is. iWatt makes no warranties with respect to this information and disclaims any implied warranties of merchantability or non-infringement of third-party intellectual property rights.

iWatt cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in an iWatt product. No circuit patent licenses are implied.

Certain applications using semiconductor products may involve potential risks of death, personal injury, or severe property or environmental damage ("Critical Applications").

iWATT SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR OTHER CRITICAL APPLICATIONS.

Inclusion of iWatt products in critical applications is understood to be fully at the risk of the customer. Questions concerning potential risk applications should be directed to iWatt Inc.

iWatt semiconductors are typically used in power supplies in which high voltages are present during operation. High-voltage safety precautions should be observed in design and operation to minimize the chance of injury.